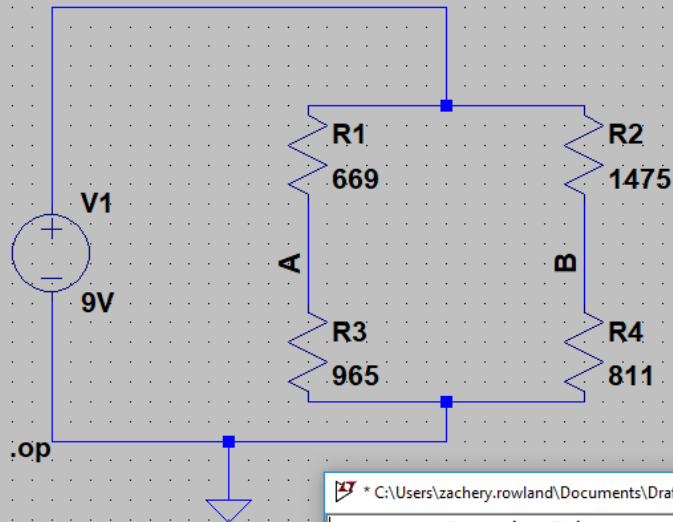



Original circuit



* C:\Users\zachery.rowland\Documents\Draft1.asc


--- Operating Point ---		
V(n001):	9	voltage
V(a):	5.31518	voltage
V(b):	3.19291	voltage
I(R4):	0.00393701	device_current
I(R2):	0.00393701	device_current
I(R3):	0.00550796	device_current
I(R1):	0.00550796	device_current
I(V1):	-0.00944496	device_current

Thevanin Equivalent

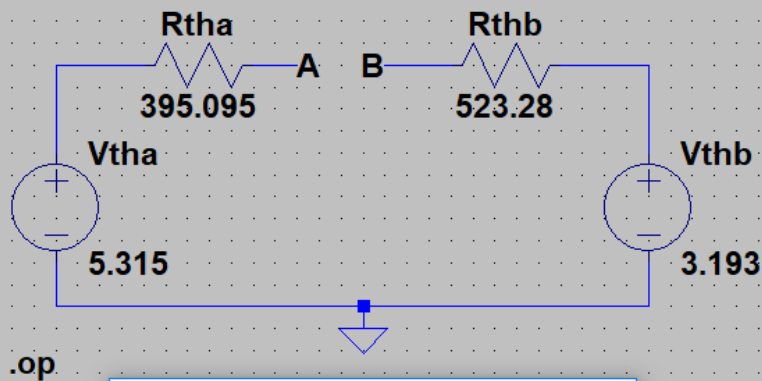

* C:\Users\zachery.rowland\Documents\Draft2.asc

--- Operating Point ---		
V(n001):	5.315	voltage
V(n002):	3.193	voltage
V(a):	5.315	voltage
V(b):	3.193	voltage
I(Rthb):	0	device_current
I(Rtha):	-2.24801e-018	device_current
I(Vthb):	0	device_current
I(Vtha):	-1.73472e-018	device_current

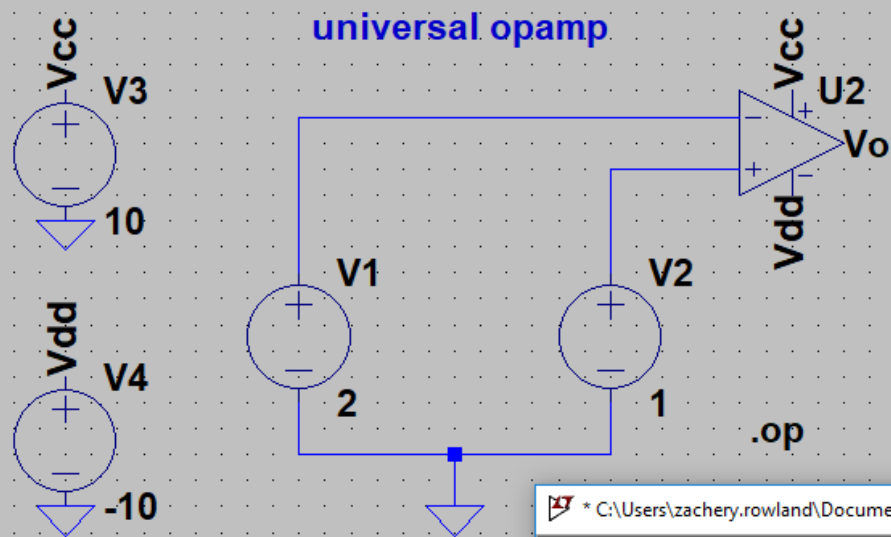

* C:\Users\zachery.rowland\Documents\Draft3.asc

--- Operating Point ---		
V(vcc):	10	voltage
V(vdd):	-10	voltage
V(n001):	2	voltage
V(n002):	1	voltage
V(vo):	-9.99998	voltage
I(V2):	-2e-009	device_current
I(V1):	-4e-009	device_current
I(V4):	2.18188e-006	device_current
I(V3):	-2.32588e-006	device_current
Ix(u2:1):	2e-009	subckt_current
Ix(u2:2):	4e-009	subckt_current
Ix(u2:3):	2.32588e-006	subckt_current
Ix(u2:4):	-2.18188e-006	subckt_current
Ix(u2:5):	1.92266e-016	subckt_current